
Lab 1: Writing a SystemVerilog Test Bench

In this lab, you have been handed a device and a specification. Your job is to make sure that the device matches the specification using a SystemVerilog test bench. The test bench has been assembled for you. You just need to provide the testing functionality.

The Device under Test

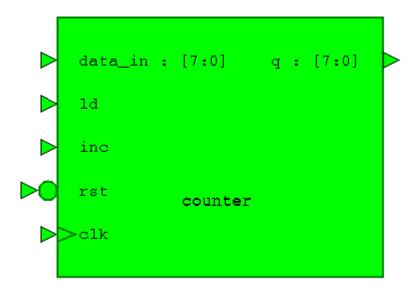The device under test (DUT) is a simple 8-bit counter. It has the following symbols and signal behavior:



- clk The counter clock.
- rst A synchronous reset
- data_in[7:0] An 8-bit bus input
- q [7:0] An 8-bit bus output
- inc -q moves to 1 q+1 on the next clock cycle if inc is 1. If q is 8'hFF it wraps around to 8'h00.
- ld -q is set equal to data_in if ld is 1. ld takes precedence over inc

Lab Assignment

- Create a test bench that proves that this design works as expected. You should be able to demonstrate that the design works to a third party.
- The test bench has already been wired up and there is a compile script in place. There are three files in the lab directory:
- run.do This script compiles the DUT and the test bench.

- DUT.sv This SystemVerilog file contains the device under test. We are treating this file as a black box, so it is not human readable.
- top.sv This is the test bench. It instantiates the DUT.

You will create your test bench in top.sv. The top.sv file looks like this:

The DUT is instantiated, and you can assign values to the clk, inc, ld, rst, and data_in signals using any combination of always and initial blocks that will test the design.

This design compiles and simulates in ModelSim or Questa using the run.do script. Use this test bench to demonstrate that the design works as described.

Extra Credit

Create a test bench that demonstrates that the design works without human intervention. That is, it runs a test or set of tests and returns a status.